

20/12/22

classmate

Date

Page


UNIT-3

OPERATIONAL AMPLIFIERS

Ques:- What is an operational amplifier? Draw & explain its block diagram. Write the characteristics of an ideal operational amplifier.

Ans:- • OP-AMP is a direct coupled high gain amplifier which can be used to amplify as well as AC signals.

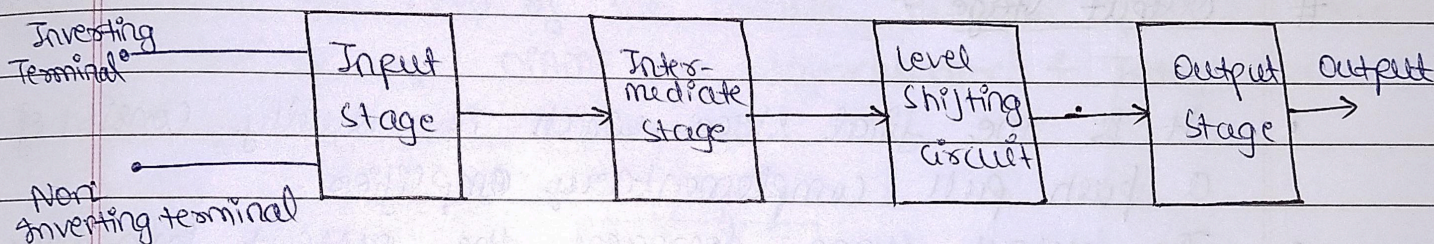- It is mainly used for mathematical operation like addition, subtraction, integration, differentiation, etc.



Input Stage -

- The input stage is the dual input balance output (DIBO) differential amplifier.
- Its function is to amplify the difference between two input signals.
- It provides high differential gain, high input impedance.

Intermediate Stage :-

- The overall gain requirement of an op-amp is very high. Intermediate stage is used to provide the required additional gain.

- It consists of another differential amplifier with dual input and unbalanced (single ended) output.


Level Shifting :-

- As the op-amp amplifies dc signal also, the small dc voltage level of previous stage may get amplified and applied as the input to the next stage causing distortion in the final output.
- So, level shifting circuit is used to bring-down the dc level to ground potential.

Output Stage :-

- It is the final stage which usually consists of a push-pull complementary amplifier.
- The output stage decreases the output impedance and increases the current supplying capability of the op-amp.

Characteristics :-

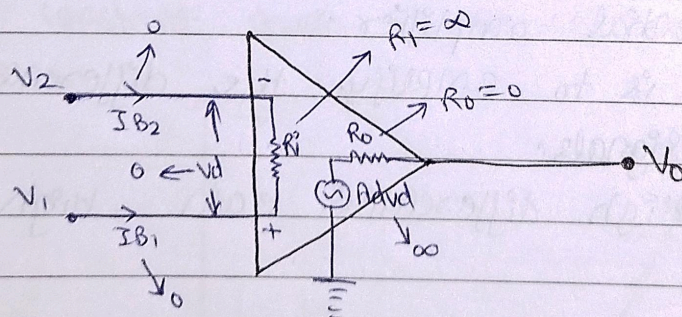


- open loop gain should be infinite
 $A_d (A_{VOL}) = \infty$
- Input resistance should be infinite.
 $R_i = \infty$

- (iii) Slew rate should be infinite
 $SR = \infty$
- (iv) CMRR should be infinite
 $CMRR = \infty$
- (v) Input offset voltage should be zero
 $V_{IO} = 0$
- (vi) Input offset current should be zero
 $I_{IO} = 0$
- (vii) Input bias current should be zero.
 $I_B = 0$

Ques 2:- With the help of the circuit diagram explain the working of OPAMP as differentiator & Integrator.

Ans:- OP-AMP as Integrator.

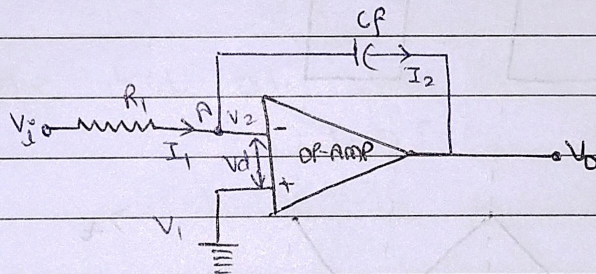

Expression for O/P -

Here $V_1 = 0$ — (1)

from concept of Virtual ground

$$V_d = 0$$

$$V_1 - V_2 = 0$$

$$V_1 = V_2$$

$$[V_1 = 0]$$

$$\therefore V_2 = 0 \quad \text{--- (2)}$$

Apply KCL at Node A

$$I_1 = I_2$$

$$\frac{V_i - V_2}{R_1} = C_f \frac{d(V_2 - V_o)}{dt}$$

but $V_2 = 0$

$$\frac{V_i}{R_1} = C \frac{d(-V_o)}{dt}$$

$$dV_o = -\frac{1}{R_1 C} V_i dt$$


now, Apply integration both sides

$$\int dV_o = -\int \frac{1}{R_1 C} V_i dt$$

$$V_o = -\frac{1}{R_1 C} \int_0^t V_i dt$$

$$V_o \propto \int_0^t V_i dt$$

I / o

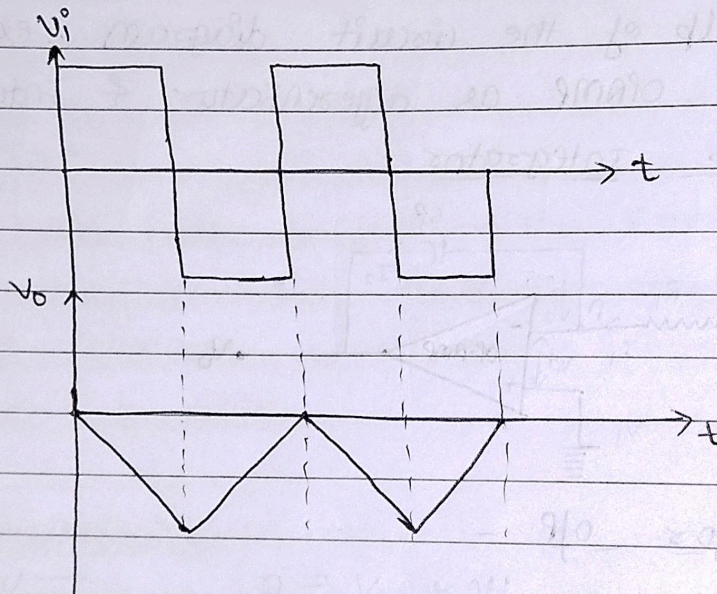


⇒ A circuit that perform the integration of input signal is called integrator. Since, the output voltage is directly proportional to the integration of input signal, Hence circuit is called integrator circuit.

Applications :-

- Used for generating triangular waves, as a low pass filter.
- Used in D to A (Digital to analog) converter circuit.

OP-AMP as a Differentiator -

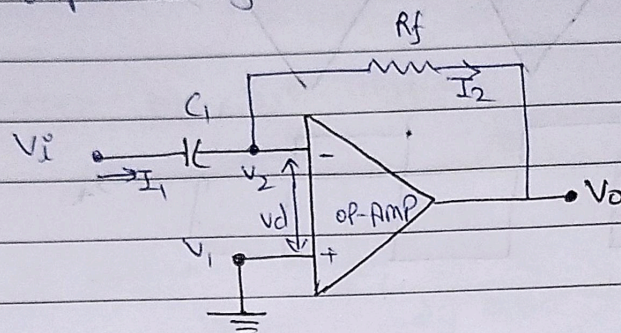A circuit that performs the mathematical differentiation of input signal is called differentiator.



Expression for o/p voltage

Here $V_1 = 0$

from concept of virtual ground, $V_d = 0$

$$V_1 - V_2 = 0$$

$$V_1 = V_2$$

$$\therefore (V_1 = 0)$$

$$\therefore V_2 = 0$$

Apply KCL at Node A

$$I_1 = I_2$$

$$C_1 \frac{d(V_i - V_2)}{dt} = \frac{V_2 - V_o}{R_f}$$

$$C_1 \frac{dV_i}{dt} = -\frac{V_o}{R_f}$$

$$V_o = -R_f C_1 \frac{dV_i}{dt}$$

$$V_o \propto \frac{dV_i}{dt}$$


Since output voltage is directly proportional to the differentiation of input signal so circuit is called differentiator circuit.

#

Application :-


- Used in high pass filter
- Used in generating square waves.
- Used in A to D converter circuit.

Input, output waveform -

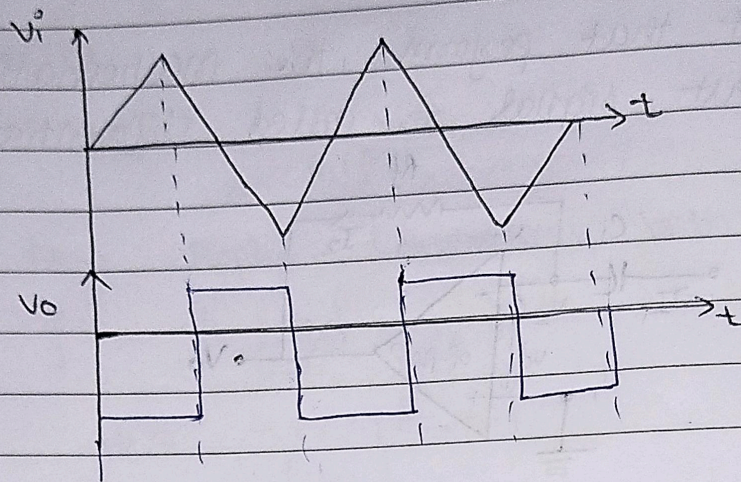

Ques 3:- Draw the subtractor & Adder using op-amp and explain its working.

Ans:- Summing or Adder Amplifiers -

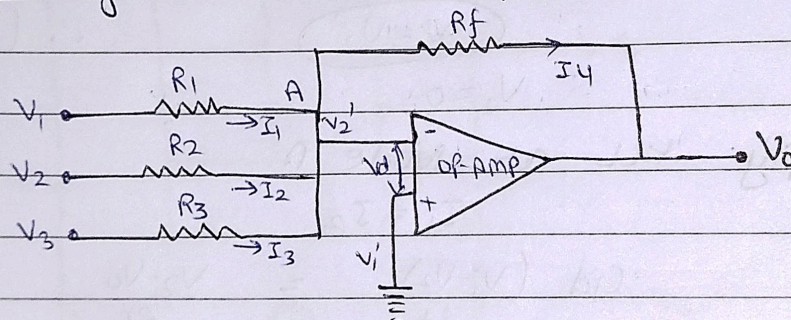

It is an op-amp circuit which can accept two or more inputs and produce output as the sum of these inputs.

Expression for o/p - $V_1' = 0$ — (1)
from concept of virtual ground

$$V_1' - V_2' = 0$$

$$\therefore V_1' = V_2' = 0 \quad \text{--- (2)}$$

Apply KCL at Node A

$$I_1 + I_2 + I_3 = I_4$$


$$\frac{V_1 - V_2'}{R_1} + \frac{V_2 - V_2'}{R_2} + \frac{V_3 - V_2'}{R_3} = \frac{V_2' - V_0}{R_f}$$

$$\text{But } V_2' = 0$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} = -\frac{V_o}{R_f}$$

$$V_o = - \left[\frac{R_f V_1}{R_1} + \frac{R_f V_2}{R_2} + \frac{R_f V_3}{R_3} \right]$$

Difference or Subtractor Amplifier -

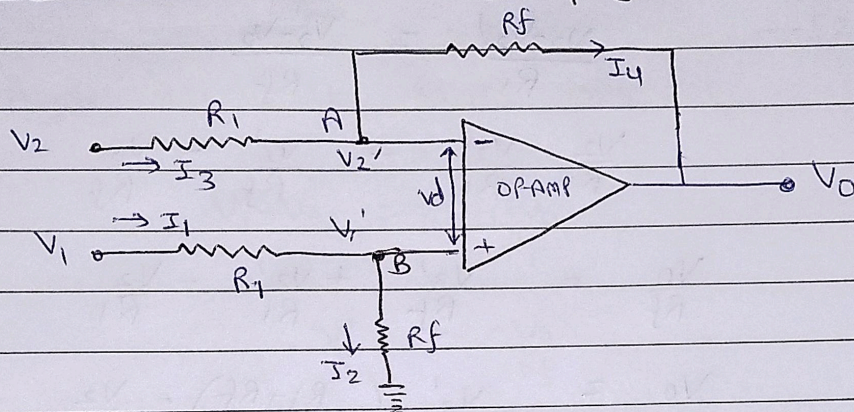

Expression for o/p voltage.

A circuit that amplifies the difference b/w two input signals is called difference / subtractor amplifier.

Expression for o/p voltage -

Apply KCL at Node B

$$I_1 = I_2$$

$$\frac{V_1 - V_1'}{R_1} = \frac{V_1' - 0}{R_f}$$

$$\frac{V_1}{R_1} = \frac{V_1'}{R_f} + \frac{V_1'}{R_f}$$

$$\frac{V_1}{R_1} = V_1' \left(\frac{R_1 + R_f}{R_f R_1} \right)$$

$$V_1' = \frac{V_1 (R_f R_1)}{R_1 (R_1 + R_f)}$$

$$V_1' = \frac{V_1 (R_f)}{(R_1 + R_f)} \quad \text{--- (i)}$$

from concept of virtual ground

$$V_d = 0$$

$$V_1 - V_2' = 0$$

$$V_1' = V_2'$$

Apply KCL at Node A

$$I_3 = I_4$$

$$\frac{V_2 - V_2'}{R_1} = \frac{V_2' - V_o}{R_f}$$

$$\frac{V_2}{R_1} - \frac{V_2'}{R_1} = \frac{V_2'}{R_f} - \frac{V_o}{R_f}$$

$$\frac{V_o}{R_f} = \frac{V_2'}{R_f} + \frac{V_2'}{R_1} - \frac{V_2}{R_1}$$

$$\frac{V_o}{R_f} = V_2' \left(\frac{R_1 + R_f}{R_f R_1} \right) - \frac{V_2}{R_1}$$

But $V_1' = V_2'$

$$\frac{V_o}{R_f} = \left(\frac{R_f}{R_1 + R_f} \right) V_1 \left(\frac{R_1 + R_f}{R_f R_1} \right) - \frac{V_2}{R_1}$$

$$V_o = \frac{R_f}{R_1} [V_1 - V_2]$$

If $R_1 = R_f$


$$V_o = V_1 - V_2$$

Ques:-

Derive the expression for gain of OP-AMP as non-inverting & Inverting amplifier.

Ans:-

Inverting Amplifier -

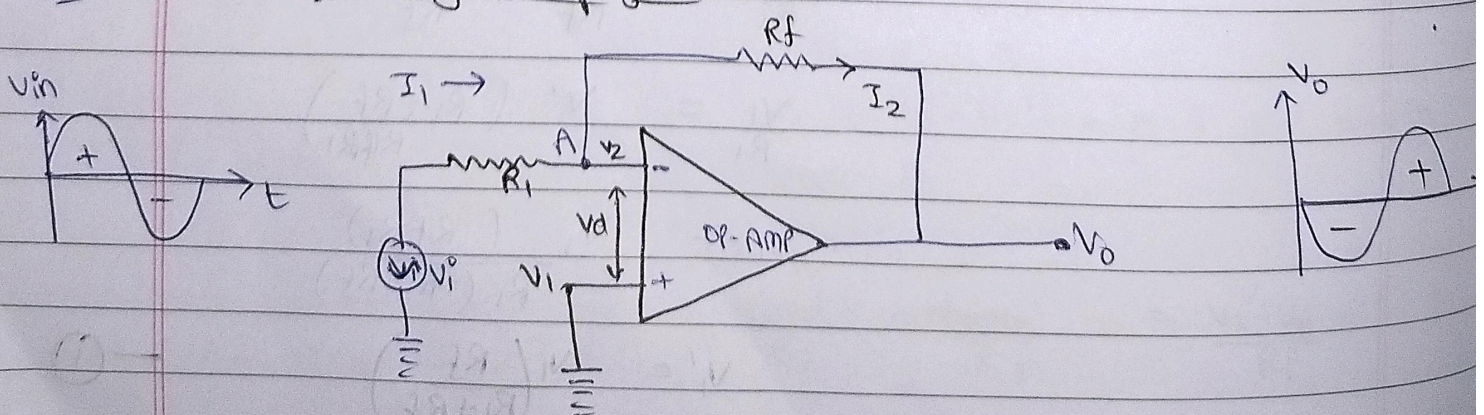

Expression for o/p voltage

Here $V_1 = 0$

— (1)

from concept of virtual ground $V_d = 0$

$$V_1 - V_2 = 0$$

$$V_1 = V_2$$

But $V_1 = 0$

$$\therefore V_2 = 0$$

— (2)

Apply KCL at Node A

$$I_1 = I_2$$

$$\frac{V_i - V_2}{R_1} = \frac{V_2 - V_o}{R_f}$$

$$\frac{V_i}{R_1} = -\frac{V_o}{R_f}$$


$$A_v = \frac{-V_o}{V_i} = -\frac{R_f}{R_1}$$

⇒ -ive sign denotes a 180° phase difference with I/P & o/p.

An op-amp circuit that produce an amplify output signal i.e. 180° out of phase with input signal.

#

Non-Inverting Amplifier

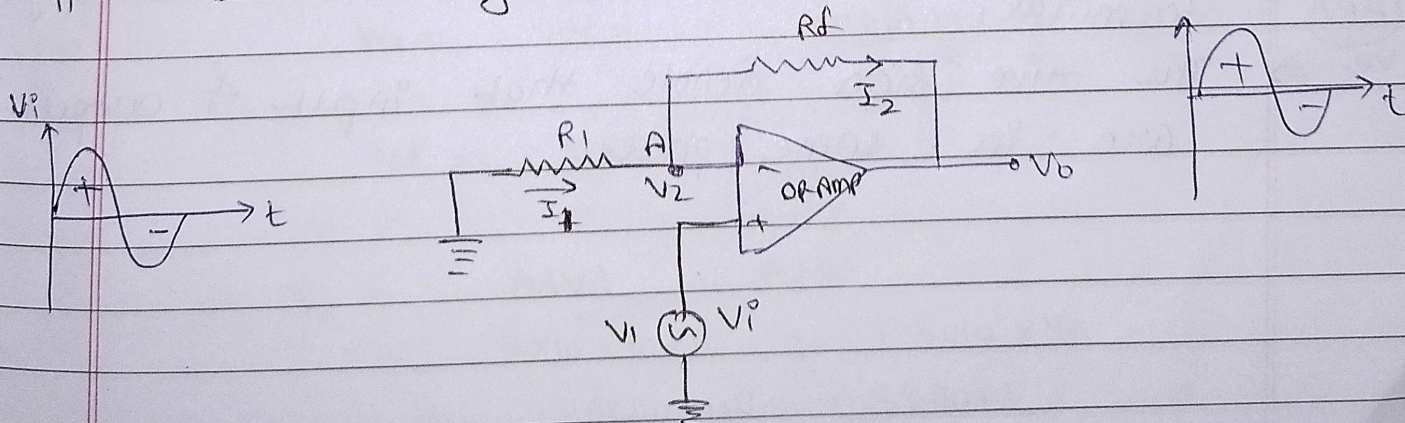

Expression for o/p voltage $V_1 = V_i$
from concept of virtual ground $V_d = 0$

$$V_1 - V_2 = 0, \quad V_1 = V_2$$

$$\text{But } V_1 = V_i \\ \therefore V_2 = V_i$$

Apply KCL at Node A

$$I_1 = I_2$$

$$\frac{V_d (V_i) - V_2}{R_1} = \frac{V_2 - V_o}{R_f}$$

$$\frac{0 - V_2}{R_1} = \frac{V_2 - V_o}{R_f}$$

$$V_2 = V_i$$

$$-\frac{V_i}{R_1} = \frac{V_i - V_o}{R_f}$$

$$\frac{V_o}{R_f} = \frac{V_i}{R_f} + \frac{V_i}{R_1}$$

$$\frac{V_o}{R_1} = \frac{R_f}{R_f} + \frac{R_f}{R_1}$$

$$A_v = \frac{V_o}{V_i} = 1 + \frac{R_f}{R_1}$$

⇒ A non-inverting amplifier is an op-AMP circuit design to provide +ve voltage gain. The input is directly applied to non-inverting terminal.

⇒ The +ve sign denote that input & output are in same phase.

Ques 5:- What do you mean by CMRR? Determine the output voltage of an opAMP for the input voltage of $V_1 = 150 \mu V$ and $V_2 = 140 \mu V$. The amplifier has differential gain $A_d = 4000$ and CMRR is 100.

Sol:- Common Mode Rejection Ratio (CMRR) is defined as the ratio of differential mode gain (A_d) and common mode gain A_c .

It is the ability to reject the common mode signal.

$$CMRR = \frac{A_d}{A_c}$$

$$CMRR \text{ in (dB)} = 20 \log_{10} \frac{A_d}{A_c}$$

$V_1 = 150 \mu V$
 $V_2 = 140 \mu V$
 $A_d = 4000$, $CMRR = 100$, $V_o = ?$

$$CMRR = \frac{A_d}{A_c}$$

$$100 = \frac{4000}{A_c}$$

$$A_c = 40$$

$$V_c = \frac{V_1 + V_2}{2} = \frac{150 + 140}{2} = \frac{290}{2} = 145 \mu V$$


$$V_d = (150 - 140) \mu V = 10 \mu V$$

$$\begin{aligned} V_o &= A_d V_d + A_c V_c \\ &= 4 \times 10^3 \times 10 \times 10^{-6} + 145 \times 10^{-6} \times 40 \\ &= 40000 \mu V + 5800 \mu V \\ &= 45800 \mu V \end{aligned}$$

$$V_o = 45.8 \text{ mV} \quad \underline{\underline{\text{Ans}}}$$

Ques 6:-

Determine the output of the following circuit
Given $V_1 = V_2 = 0.15 \text{ V}$.

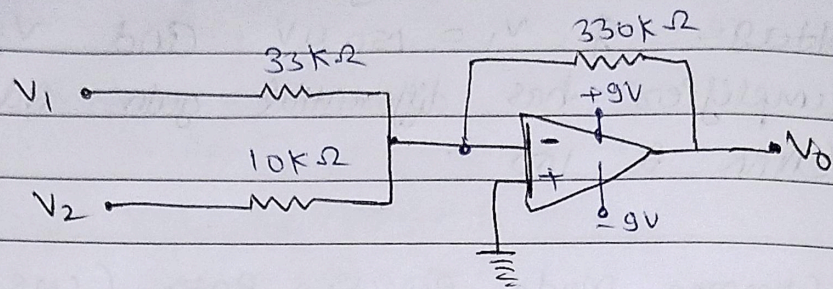Soln:-


This is a Summing or Adding amplifier

$$\begin{aligned}
 V_o &= - \left[\frac{R_f V_1}{R_1} + \frac{R_f V_2}{R_2} \right] \\
 &= - \left[\frac{330 \times 0.15}{33} + \frac{330 \times 0.15}{10} \right] \\
 &= - \left[\frac{49.5}{33} + \frac{49.5}{10} \right] \\
 V_o &= - [1.5 + 4.95]
 \end{aligned}$$

$$V_o = -6.45 \text{ V}$$

Ques 7:-

Explain the concept of virtual ground in op-amp. Determine output voltage for given network.

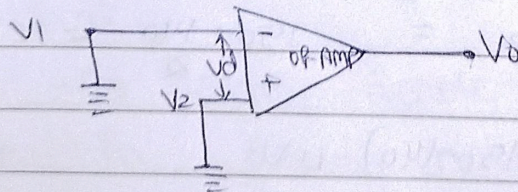Ans:-

If one terminal of op-amp is connecting to ground then another terminal will also be at ground this is called concept of virtual ground. The concept of virtual ground is used to determine closed loop voltage gain & output voltage.

For an ideal op-amp


$$R_d = \infty$$

$$V_o = A_d V_d$$

$$V_d = \frac{V_o}{R_d} = \frac{V_o}{\infty} = 0$$

$$V_1 - V_2 = 0$$

$$V_1 = V_2$$

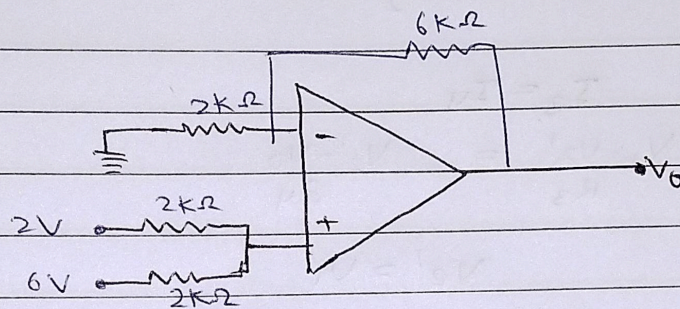

This is non-inverting adder.

$$V_o = A_{Vf} \times V_i$$


$$= \left[1 + \frac{R_f}{R_i} \right] \times \left[\frac{V_a + V_b}{2} \right]$$

$$= \left[1 + \frac{6}{2} \right] \times \left[\frac{2+6}{2} \right]$$

$$= \left[\frac{8}{2} \right] \times \frac{8}{2}$$

$$= \boxed{16 \text{ Volt}} \quad \underline{\underline{\text{Ans}}}$$

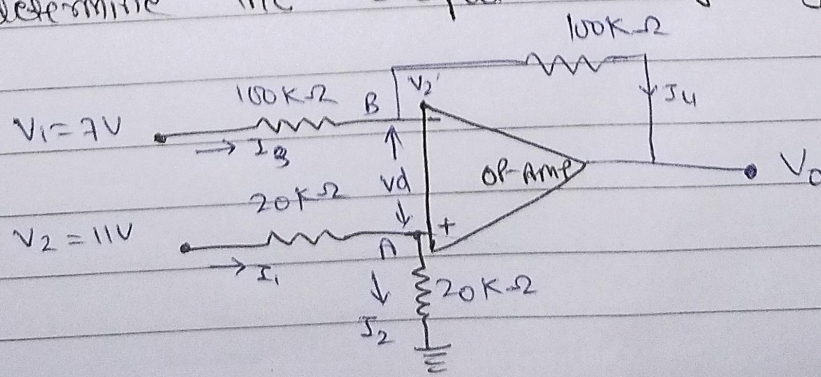Ques: Also determine the output voltage of following circuit



60/2

$$I_1 = I_2$$

$$\frac{V_2 - V_1'}{R_1} = \frac{V_1'}{R_2}$$

$$\frac{11 - V_1'}{20} = \frac{V_1'}{20}$$

$$11 - V_1' = V_1'$$

$$2V_1' = 11$$

$$V_1' = \frac{11}{2} = 5.5 \text{ K}\Omega$$

$$I_3 = I_4$$

$$\frac{V_1 - V_2'}{R_3} = \frac{V_2' - V_0}{R_4}$$

$$V_2' = V_1'$$

$$\frac{7 - 5.5}{100} = \frac{5.5 - V_0}{100}$$

$$\frac{1.5}{100} = \frac{5.5 - V_0}{100}$$

$$150 = 550 - 100V_0$$

$$+100V_0 = 550 - 150$$

$$V_0 = \frac{400}{100}$$

$$V_0 = 4V$$